

## Worksheet of Experiment

Date of Experiment	10 sep, 2024
Name	Akshada Jotiram Ghorpade.
Registration Number	12302956.

**Title of Experiment:** Develop RTL designs in verilog to implement multiplexer and demultiplexer and verify their functionality using cadence NCSIM.


**Name of Language:** Verilog.

**Name of Software:** Cadence NCSIM, simvision.

**Theory of Experiment:**
 
### **Multiplexer:**


- A multiplexer is a combinational circuit that has  $2^n$  input lines and a single output line. Simply, the multiplexer is a multi-input and single-output combinational circuit.
- The binary information is received from the input lines and directed to the output line. On the basis of the values of the selection lines, one of these data inputs will be connected to the output.



### ▪ 8 to 1 Multiplexer

- In the 8 to 1 multiplexer, there are total eight inputs, i.e.,  $A_0, A_1, A_2, A_3, A_4, A_5, A_6,$  and  $A_7$ , 3 selection lines, i.e.,  $S_0, S_1$  and  $S_2$  and single output, i.e.,  $Y$ .
- On the basis of the combination of inputs that are present at the selection lines  $S^0, S^1,$  and  $S_2$ , one of these 8 inputs are connected to the output.

**Block Diagram:**

 


Truth table:

INPUTS			Output
$S_2$	$S_1$	$S_0$	Y
0	0	0	$A_0$
0	0	1	$A_1$
0	1	0	$A_2$
0	1	1	$A_3$
1	0	0	$A_4$
1	0	1	$A_5$
1	1	0	$A_6$
1	1	1	$A_7$

Boolean expression:


$$Y = S_0' \cdot S_1' \cdot S_2' \cdot A_0 + S_0' \cdot S_1' \cdot S_2 \cdot A_1 + S_0' \cdot S_1 \cdot S_2' \cdot A_2 + S_0' \cdot S_1 \cdot S_2 \cdot A_3 + S_0 \cdot S_1' \cdot S_2' \cdot A_4 + S_0 \cdot S_1' \cdot S_2 \cdot A_5 + S_0 \cdot S_1 \cdot S_2' \cdot A_6 + S_0 \cdot S_1 \cdot S_2 \cdot A_7$$

Circuit Diagram:

 
 
## Demultiplexer:


- A De-multiplexer is a combinational circuit that has only 1 input line and  $2^N$  output lines. Simply, the multiplexer is a single-input and multi-output combinational circuit.
- The information is received from the single input lines and directed to the output line. On the basis of the values of the selection lines, the input will be connected to one of these outputs.



## 1×4 De-multiplexer:

- In 1 to 4 De-multiplexer, there are total of four outputs, i.e.,  $Y_0$ ,  $Y_1$ ,  $Y_2$ , and  $Y_3$ , 2 selection lines, i.e.,  $S_0$  and  $S_1$  and single input, i.e.,  $A$ .
- On the basis of the combination of inputs which are present at the selection lines  $S_0$  and  $S_1$ , the input be connected to one of the outputs.

### Block Diagram:

 


### Truth table

INPUTS		Output			
$S_1$	$S_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	A
0	1	0	0	A	0
1	0	0	A	0	0
1	1	A	0	0	0

**Boolean expression:**

$$\begin{aligned} Y_0 &= S_1' S_0' A \\ Y_1 &= S_1' S_0 A \\ Y_2 &= S_1 S_0' A \\ Y_3 &= S_1 S_0 A \end{aligned}$$

**Circuit Diagram:**

 

**Program and Stimulus (Testbench) program:**

**PROGRAM (Multiplexer):**

```
module mux8(i, s, y);
input [7:0] i;
input [2:0] s;
output y;
assign y=i[0]&(~s[2])&(~s[1])&(~s[0])|
        i[1]&(~s[2])&(~s[1])&(s[0])|
        i[2]&(~s[2])&(s[1])&(~s[0])|
        i[3]&(~s[2])&(s[1])&(s[0])|
        i[4]&(s[2])&(~s[1])&(~s[0])|
        i[5]&(s[2])&(~s[1])&(s[0])|
        i[6]&(s[2])&(s[1])&(~s[0])|
        i[7]&(s[2])&(s[1])&(s[0]);
endmodule
```

### **TESTBENCH (Multiplexer):**

```
module mux8tb;
reg [7:0] i;
reg [2:0] s;
wire y;
mux8 dut(i, s, y);
initial
begin
i=8' b10000000;
s=3' b000;
#10 s=3' b001;
#10 s=3' b010;
#10 s=3' b011;
#10 s=3' b100;
#10 s=3' b101;
#10 s=3' b110;
#10 s=3' b111;
#10 $stop;
end
endmodule
```

### **PROGRAM (Demultiplexer):**


```
module demux(i,s1,s0,y0,y1,y2,y3);
input i,s1,s0;
output y0,y1,y2,y3;
wire w1,w2;
not(w1,s1);
not(w2,s0);
and (y0,w1,w2,i);
and (y1,w1,s0,i);
and (y2,s1,w2,i);
and (y3,s1,s0,i);
endmodule
```

### TESTBENCH (Demultiplexer):


```
module demuxtb;  
  reg i,s1,s0;  
  wire y0,y1,y2, y3;  
  demux dut(i,s1,s0,y0,y1,y2,y3);  
  initial  
  begin  
    i=1;  
    s1=0;s0=0;  
    #10 s1=0;s0=1;  
    #10 s1=1;s0=0;  
    #10 s1=1;s0=1;  
    #10 $stop;  
  end  
endmodule
```

### Simulation waveform:

#### Multiplexer

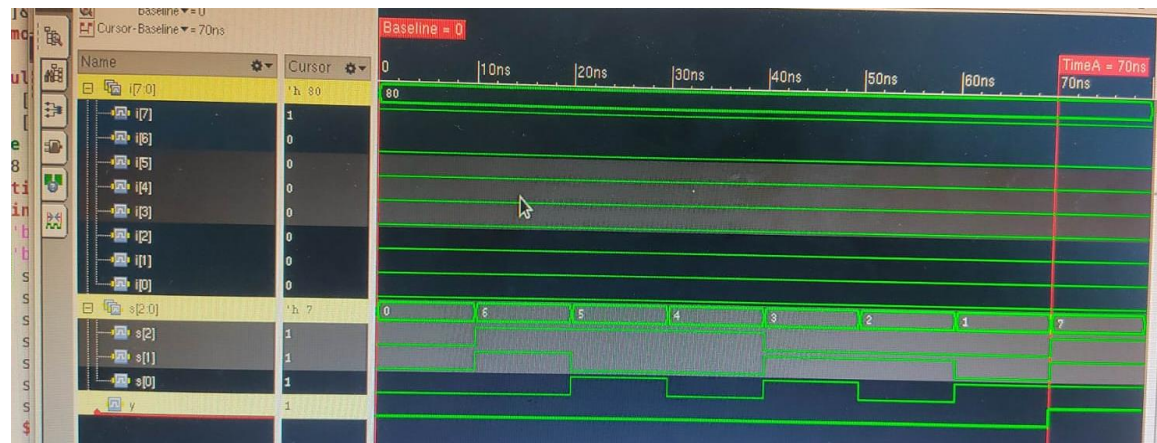


#### Demultiplexer

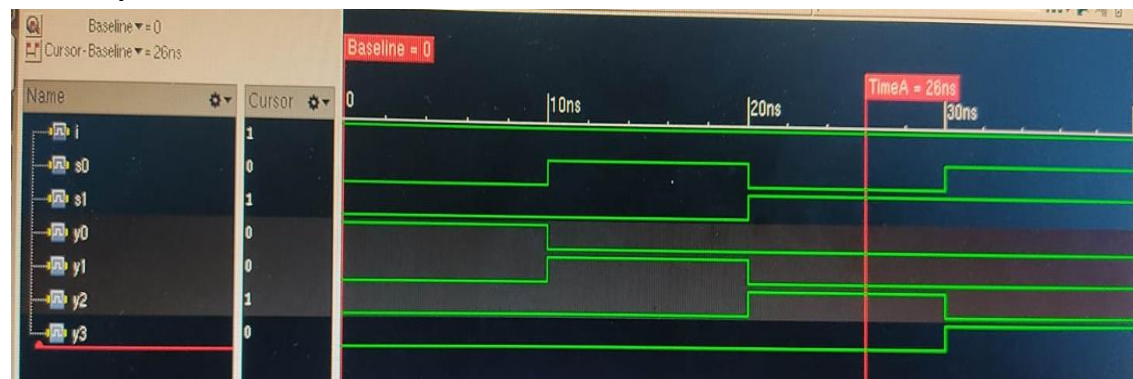


## RTL Schematic:

### Multiplexer

 

### Demultiplexer

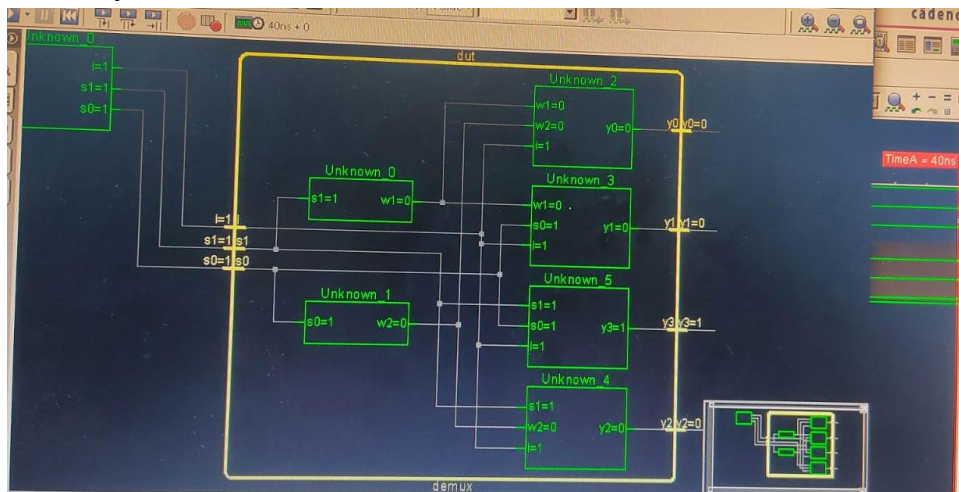

## Learning Outcome:

1. Learn to write syntactically correct Verilog code for multiplexer and demultiplexer.
2. Create testbenches to simulate and verify the functionality of multiplexer and demultiplexer.
3. Apply techniques to optimize logic circuits for speed, area, and power efficiency.
4. Perform timing analysis to ensure circuits meet required timing constraints.
5. Analyze the performance of multiplexer and demultiplexer and circuits in terms of timing, power, and area using simulation results.





